


POST LAB FOR LAB 6

ECEN 350

Chenjie Luo


324007289

## 1. Half adder

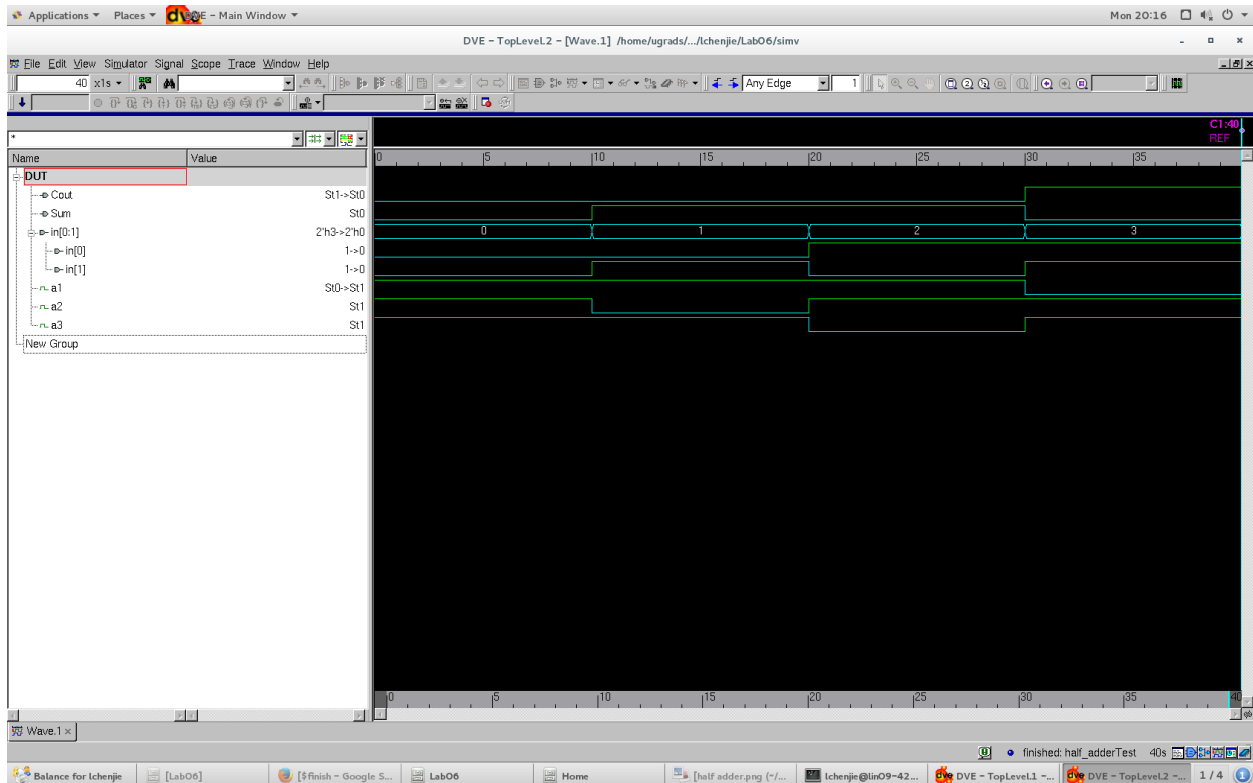


Half adder basically realizes the addition function. The output contains 2 bits. One is Sum, which represent the sum, another one is Cout, which represents the Carry. Using the Boolean algebra, we know:  $\text{Sum} = \text{in}[0] \oplus \text{in}[1]$ . Because the lab manual requires using NAND gate only,  $\text{Sum} = (((\text{in}[0] * \text{in}[1])' * \text{in}[1]) * ((\text{in}[0] * \text{in}[1])' * \text{in}[0]))'$  and  $\text{Cout} = ((\text{in}[0] * \text{in}[1])' * (\text{in}[0] * \text{in}[1]))'$

## 2. Mux:

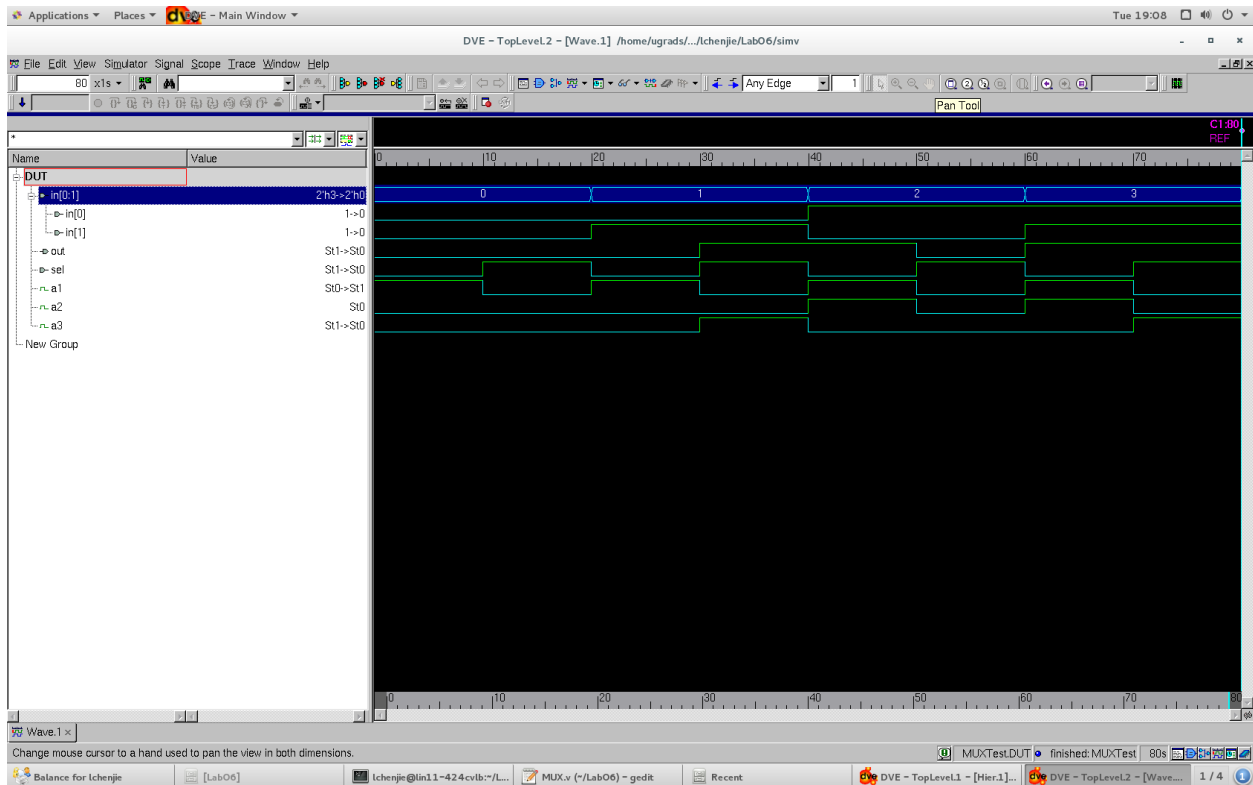

Multiplexer works as the function:  $\text{output} = \text{in}[0] * \text{sel} + \text{in}[1] * \text{sel}$ . Basically, it will decide which bit to transfer according to its input sel. For example, when sel is 0,  $\text{output} = \text{in}[0]$ . Similarly, when sel is 1,  $\text{output} = \text{in}[1]$ .

### 3. 2-4 decoder

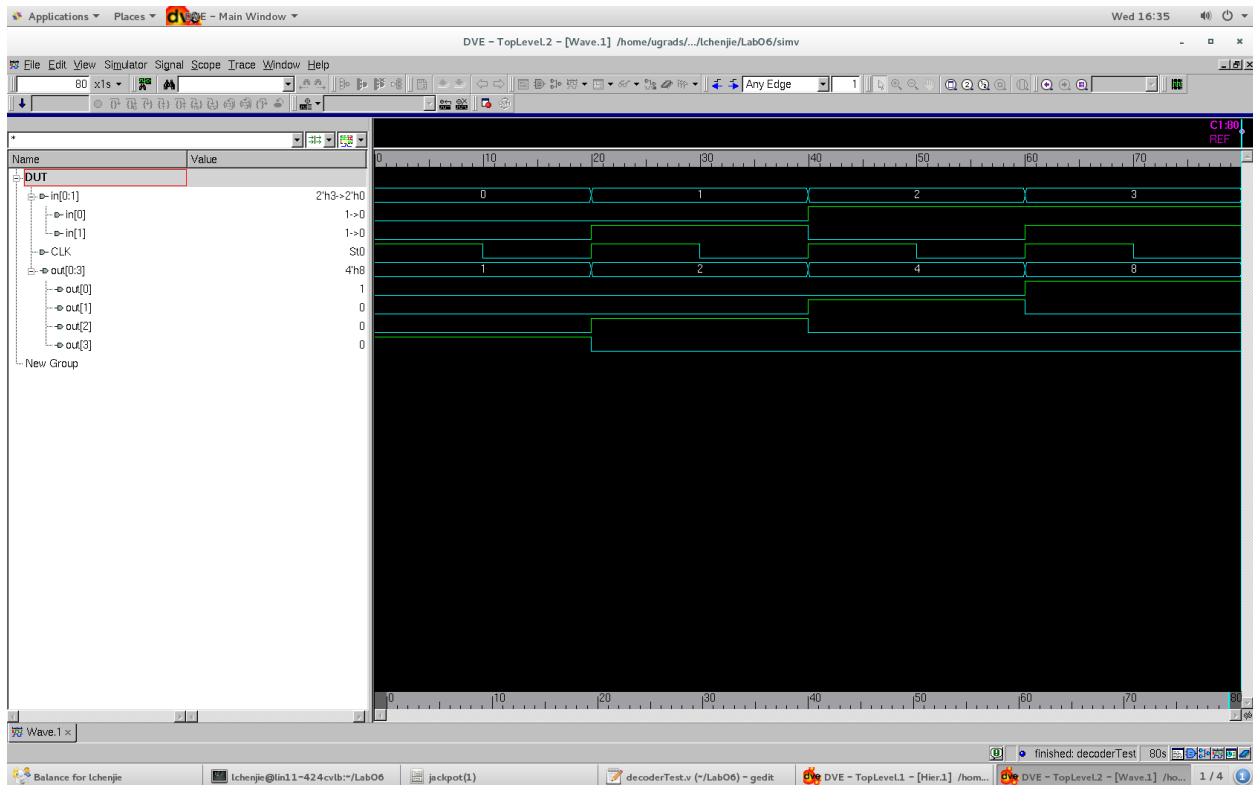

2-4 decoder works for the function that illustrates which output input is representing. 2 stands for 2-bit input and 4 stands for 4-bit output. For example, if input = 2'b 00, it means second bit is what input represents so now output is 4'b0001.

Similarly,

input = 2'b01, output = 4'b0010;

input = 2'b10, output = 4'b0100;

input = 2'b11, output = 4'b1000;